

8 - Oct - 2020

## Elec mimos

### Diodes models


A model is a way of describing the behaviour of a system by using a mathematical formula or a schematic simplification.


→ We have two diode models which means that we have two ways to approximate how a diode functions.
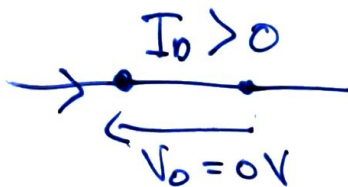
#### 1. The ideal model


\* Here the diode is assumed to be a perfect switch



Forward bias :  (closed switch)

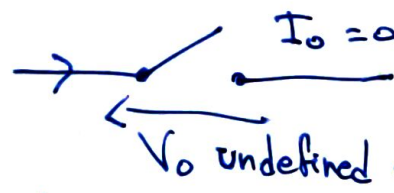Reverse bias :  (open switch)

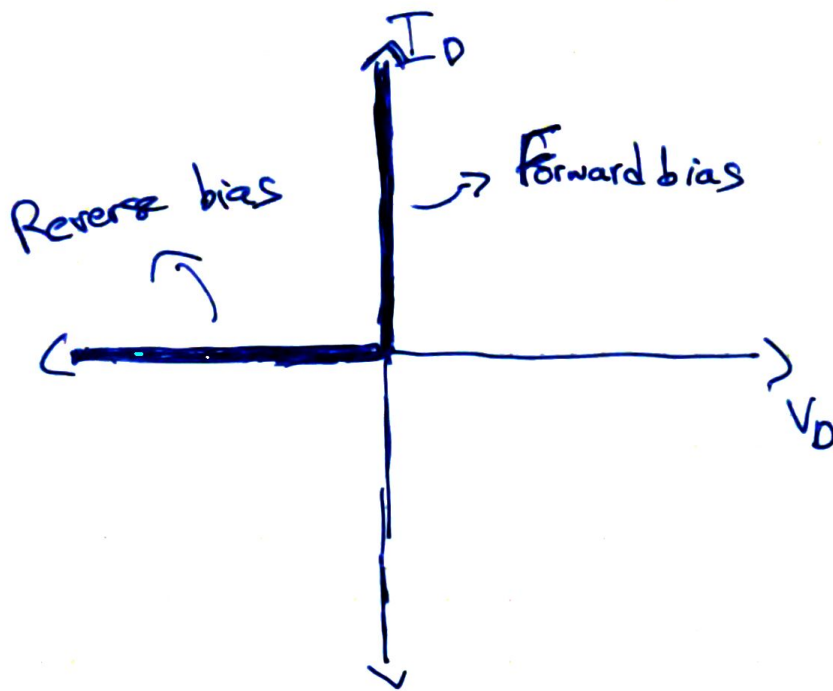\* Most used model, especially power applications where voltage varies from tens to thousands.



## 2. The threshold model


- We have a threshold voltage ( $V_0$ ) for conduction
- The threshold voltage depends on the diode material

Silicon:  $V_0 = 0.7$



Germanium:  $V_0 = 0.3$

- Used for low voltages.
- Diode is approximated to a voltage source + a switch

Forward bias:

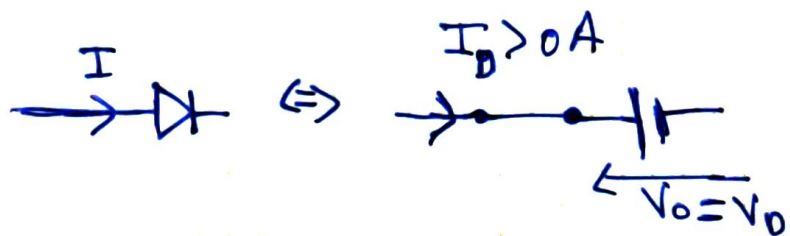


Reverse bias:

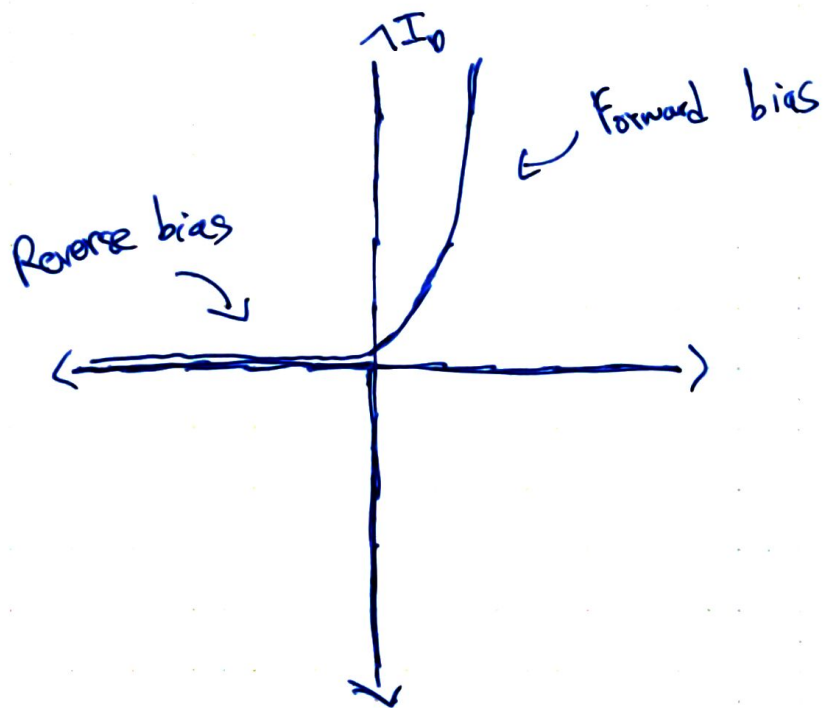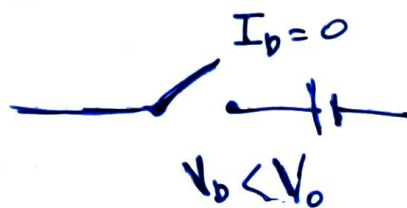

### Example:

\* Determine if the diode is conducting or not,  
if conducting, calculate  $I_D$

Use threshold model with  $V_0 = 0.7V$

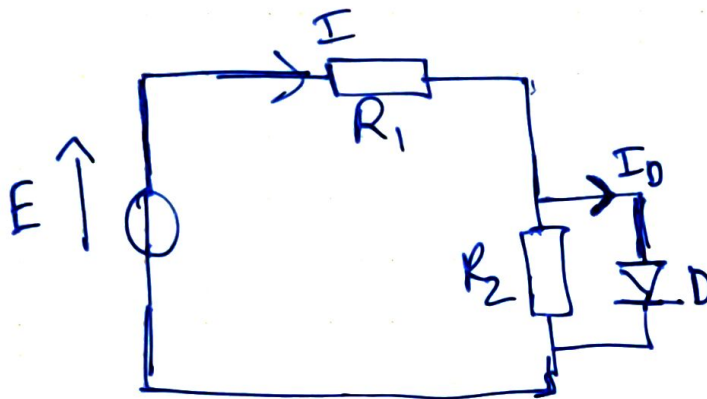


$$E = 10V$$

$$R_1 = 100\Omega$$

$$R_2 = 40\Omega$$

We assume that  $D$  is not conducting  
which means  $I_D = 0$  and  $V_D < V_0$


(Proof  
by  
contradiction)

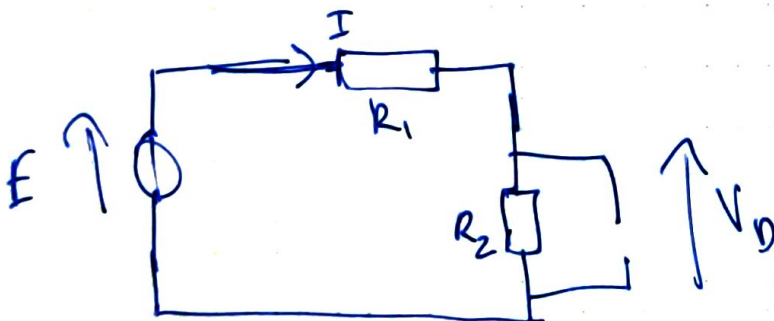

$$V_D = \frac{ER_2}{R_1 + R_2} = \frac{400}{140} = 2.85V$$

But  $V_D > V_0$   $\therefore$  It is conducting  
(assumption is wrong)

For  $I_D \Rightarrow$

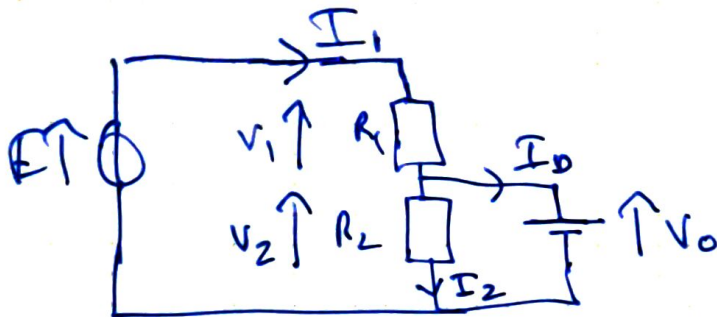

$$\begin{aligned} V_2 &= V_0 \\ E - v_1 - v_2 &= 0 \end{aligned} \quad \left. \vphantom{\begin{aligned} V_2 &= V_0 \\ E - v_1 - v_2 &= 0 \end{aligned}} \right\} \text{KVL}$$

$$I_1 - I_2 = I_D$$

$$V_1 = E - V_2 = E - V_0 = R_1 I_1$$

$$\Rightarrow I_1 = \frac{E - V_0}{R_1}$$

$$V_2 = R_2 I_2 = V_0$$

$$\Rightarrow I_2 = \frac{V_0}{R_2}$$

$$\begin{aligned} \therefore I_D &= \frac{E - V_0}{R_1} - \frac{V_0}{R_2} = \frac{10 - 0.7}{100} - \frac{0.7}{40} \\ &= 75.5 \text{ mA} \end{aligned}$$