




## Tutorial 0: Revision
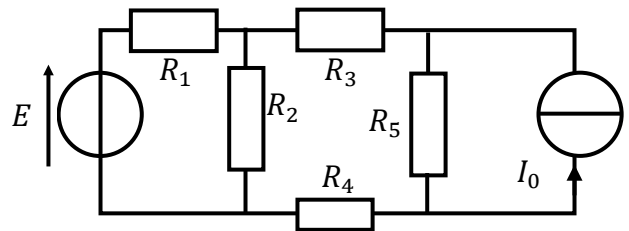
### Exercise 1

Consider the network opposite. We have

- $E = 10V, I_0 = 10mA$
- $R_1 = 1k\Omega, R_2 = 1,2k\Omega, R_3 = 500\Omega,$   
 $R_4 = 1,5k\Omega, R_5 = 2k\Omega$




Determine the Thévenin generator seen by  $R_2$ . You will use the method of your choice (Equivalences or application of the theorem), and you will express your result as a function of  $I_0, E$  and resistances.

Deduce the voltage across  $R_2$

### Exercise 2

Consider the circuit opposite.


$E_1, E_2, I$  and  $R$  are assumed to be known, and the generators are independent. Determine the expression of the voltage  $U$  using the method which seems most appropriate to you (Kirchhoff's laws, superposition, Thévenin, Norton or Millman theorem), indicating it beforehand.

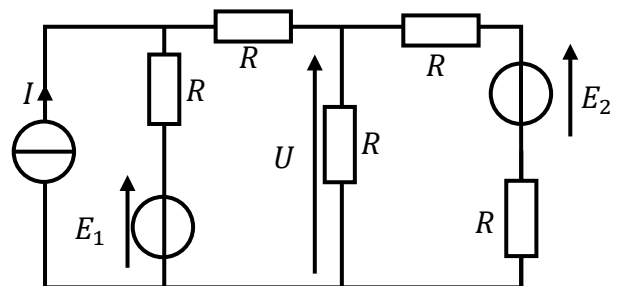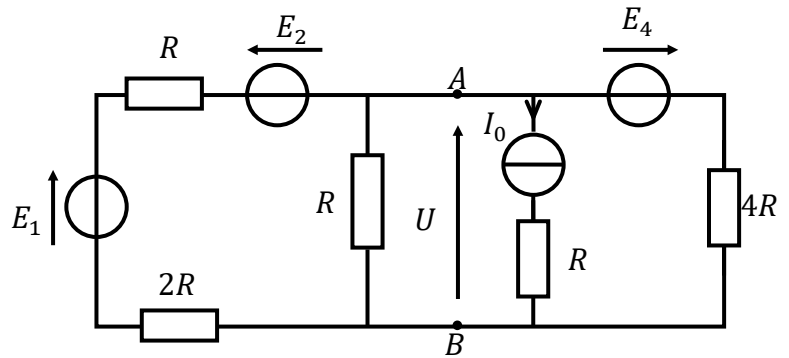

Exercise 3

Consider the network opposite.

Determine the expression of the voltage  $U$  using the method that seems the most appropriate (Kirchhoff's laws, superposition theorem, Thévenin, Norton or Millman theorem), indicating it beforehand. You will express  $U$  as a function of  $E_1$ ,  $E_2$ ,  $E_4$ ,  $I_0$  and resistances  $R$ .

Exercise 4

Consider the network opposite.  
Determine  $U$ .

