

Memo

Reminders from last year :-

• Thevenin's Theorem :-

Goal: Replace a complex network by a ~~comp~~ simple one



* Finding R_{th}

- Remove R^*
- Remove all the sources
- $R_{th} = R_{eq}$

* Finding E_{th}


- Put back sources
- $E_{th} = U_{AB}$

Example:

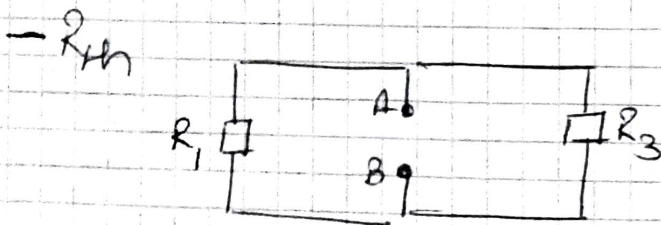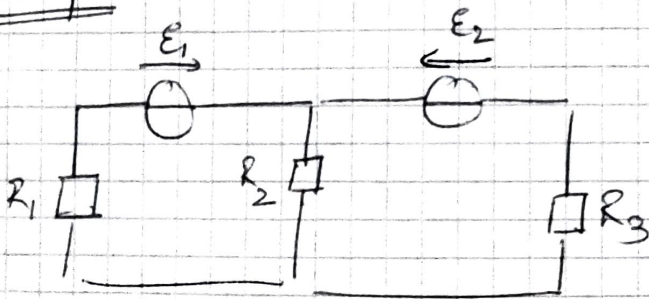


We assume A and B are two terminals
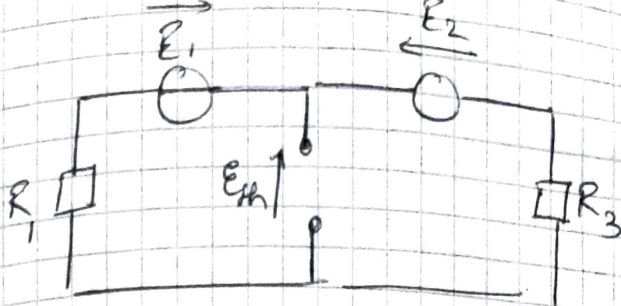
$$R_{th} = \frac{R_1 \times R_3}{R_1 + R_3}$$




Using superposition:

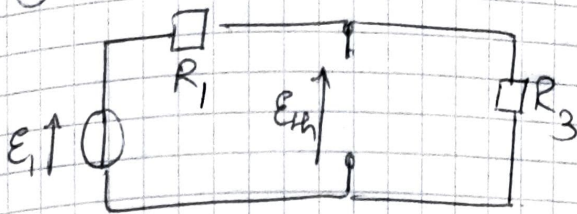

$$E_{th} = V_3 \text{ (both are in parallel)}$$

(By calculation)
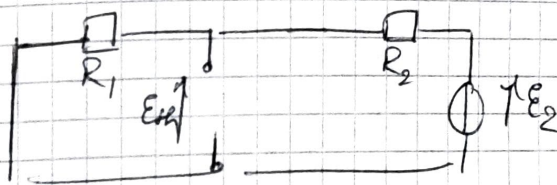
$$V_3 = \frac{E_1 R_3}{R_1 + R_3} = E_{th1} \quad \text{--- (I)}$$



$$E_{th} = V_1$$


$$V_1 = \frac{E_2 R_1}{R_1 + R_3} = E_{th2} \quad \text{--- (II)}$$

Add (I) and (II)

$$E_{th} = E_{th1} + E_{th2}$$

$$E_{th} = \frac{1}{R_1 + R_3} (E_2 R_1 + E_1 R_3)$$

Theremin generator
across R_2

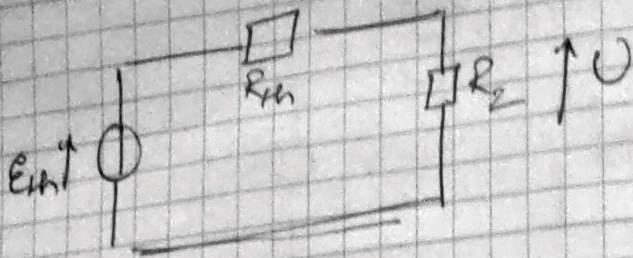

$$U = \frac{E_{th} R_2}{R_{th} + R_2}$$

$$U = \frac{E_2 R_1 + E_1 R_3}{R_1 + R_3} \times \frac{R_2}{\frac{R_1 R_3}{R_1 + R_3} + R_2}$$

$$= \frac{E_2 R_1 + E_1 R_3}{R_1 + R_3} \times \frac{R_2 (R_1 + R_3)}{R_1 R_3 + R_2 (R_1 + R_3)}$$

$$U = \frac{R_2 (E_2 R_1 + E_1 R_3)}{R_2 (R_1 + R_3) + R_1 R_3}$$

• Norton Theorem :-

Goal : Same as Thevenin

* Finding R_N

— Remove R

— Remove all the sources


— $R_{eq} = R_N$

* Finding I_N

— Put back sources

— Short circuit the branch


Ex:

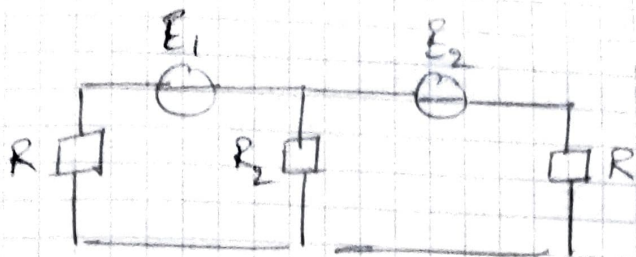


$-R_N$

$$R_{Th} = R_N = \frac{R}{2}$$

$-I_N$

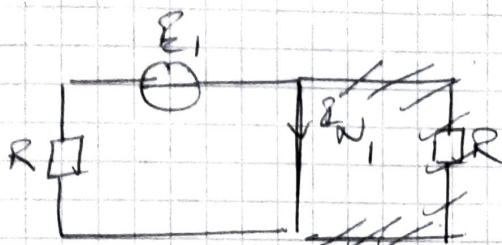

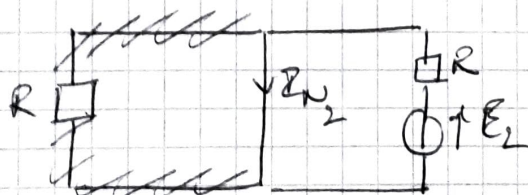
$$I_{N1} = \frac{E_1}{R} \quad \text{--- (i)}$$



$$I_{N2} = \frac{E_2}{R} \quad \text{--- (ii)}$$
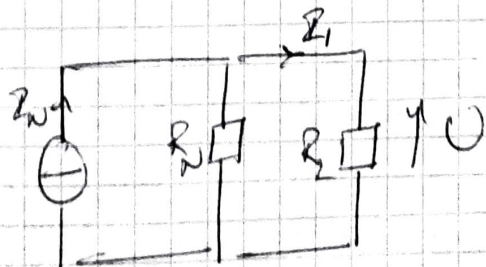
$$I_N = \frac{E_1}{R} + \frac{E_2}{R} = \frac{E_1 + E_2}{R}$$



$$I_1 = \frac{I_N R_N}{R_N + R_2}$$

$$U = \frac{I_N R_N \times R_2}{R_N + R_2}$$


• Newton and Thevenin equivalence

$$E_m = I_N \times R_N$$

$$I_N = \frac{E_m}{R_m}$$

$$(R_m = R_N)$$

• Millman Theorem

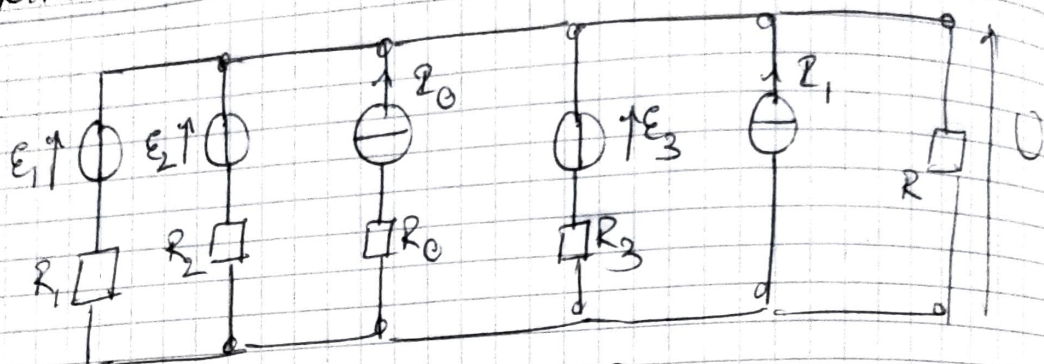

$$V = \frac{\sum_{i=1}^n \frac{E_i}{R_i} + \sum_{k=1}^p I_k}{\sum \frac{1}{R_i}}$$

$$V = \frac{\frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3} + I_0 + I_1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R}}$$

$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R}$ (Include all the resistances except the one which are in series with current source)

Tip: Use millman when the components are in parallel.

By parallel, what I mean is, every branch having equal voltage